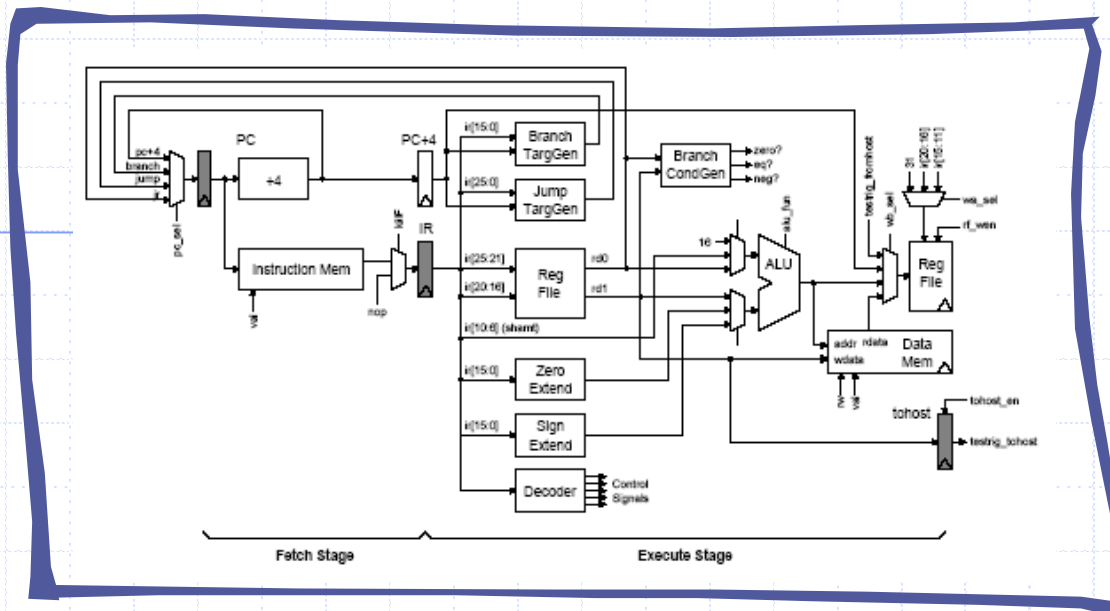


Verilog 2 - Design Examples



Modified by Michael Taylor from Arvind's MIT 6.375 slides.

Verilog can be used at several levels

High-Level Behavioral



Register Transfer Level



Gate Level

A common approach is to use C/C++ for initial behavioral modeling, and for building test rigs

automatic tools to synthesize a low-level gate-level model

Writing synthesizable Verilog

Recap: Combinational logic

- ◆ Use continuous assignments (**assign**)

```
assign C_in = B_out + 1;
```

- ◆ Use **always_comb** blocks with blocking assignments (=)

```
always_comb
begin
    out = 2'd0;
    if (in1 == 1)
        out = 2'd1;
    else if (in2 == 1)
        out = 2'd2;
end
```

always blocks allow more expressive control structures, though not all will synthesize

default value

- ◆ Every variable should have a *default value* to avoid inadvertent introduction of latches
- ◆ Don't assign to same variable from more than one **always_comb** block. Race conditions in behavioral sim, synthesizes incorrectly.

Writing synthesizable Verilog: Sequential logic

- ◆ Use `always_ff @(posedge clk)` only with non-blocking assignment operator (`<=`)

```
always_ff @(posedge clk)
    C_out <= C_in;
```

- ◆ Use only positive-edge triggered flip-flops for state
- ◆ Do not assign the same variable from more than one `always_ff` block. Race condition in behavioral simulation; synthesizes incorrectly.
- ◆ Do not mix blocking and non-blocking assignments
 - only use non-blocking assignments (`<=`) for sequential logic.
 - only use block assignments (`=`) for combinational logic.
- ◆ Like in software engineering, express your design as a module hierarchy that corresponds to logical boundaries in the design. Also, separate datapath and control (more later)

An Example: Good Style

```
wire A_next, B_next, C_next;  
reg  A_r, B_r, C_r;
```

```
always_ff @( posedge clk )  
begin
```

```
    A_r <= A_next;
```


```
    B_r <= B_next;
```

```
    C_r <= C_next;
```

```
end
```

```
assign B_next = A_r + 1;
```

```
assign C_next = B_r + 1;
```

 

Readable,
combinational and
sequential logic are
separated.


*Standard naming: A_r
is the output of the
register and A_{next}
(or A_n) is the input.*

An Example: Good Style

```
wire A_next;
reg B_next, C_next;
reg A_r, B_r, C_r;

always_ff @( posedge clk )
begin
    A_r <= A_next;
    B_r <= B_next;
    C_r <= C_next;
end

 always_comb
begin
    B_next = A_r + 1;
    C_next = B_r + 1;
end
```



Readable,
combinational and
sequential logic are
separated.

Alternate implementation?

```
wire A_next, B_next, C_next;  
reg  A_r, B_r, C_r;
```

```
always_ff @( posedge clk )  
begin
```

```
    A_r <= A_next;
```


```
    B_r <= B_next;
```

```
    C_r <= C_next;
```

```
    assign B_next = A_r + 1;
```

```
    assign C_next = B_r + 1;
```


```
end
```

 

Syntactically
Incorrect.

An Example: Okay, but less readable?
 
```
wire A_next;  
reg  A_r, B_r, C_r;  
  
always_ff @( posedge clk )  
begin  
    A_r <= A_next;  
    B_r <= A_r + 1;  
    C_r <= B_r + 1;  
end
```




Is (B_r == A_next+1) ?

Nope - Why?

A_r <= A_next creates
a register between
A_next and A_r, not a wire.

Another style – multiple always blocks
 
```
wire A_n, B_n, C_n;  
reg  A_r, B_r, C_r;  
  
always_ff @( posedge clk )  
    A_r <= A_n;  
  
assign B_n = A_r + 1;  
  
always_ff @( posedge clk )  
    B_r <= B_n;  
  
assign C_n = B_r + 1;  
  
always_ff @( posedge clk )  
    C_r <= C_n;
```




Does it have the same
functionality?

Yes. But why?

It generates the same
underlying circuit.

How about this one?
 
```
wire A_n, B_n, C_n;  
reg  A_r, B_r, C_r;  
  
always @(posedge clk )  
begin  
    A_r = A_n;  
    B_r = B_n;  
    C_r = C_n;  
end  
  
assign B_n = A_r + 1;  
assign C_n = B_r + 1;
```



Will this synthesize?

→ Maybe

Is it correct?

→ No; Do not use “blocking assignments” in @posedge clk blocks. It is forbidden in this class.

What does this do? (*This is correct but bad code.*)

```
wire B_in, C_in;
reg  A_r;
wire sel;

always @( posedge clk )
begin
    A_r <= 1'b0;
    A_r <= B_in;

    if (sel)
        A_r <= C_in;
end
```

Desugar into separate comb. and seq. logic.

```
wire B_in, C_in;
reg A_r;
wire sel;

always @( posedge clk )
begin
    A_r <= 1'b0; // redundant!
    A_r <= B_in;

    if (sel)
        A_r <= C_in;
end
```

```
wire A_n, B_in, C_in;
reg A_r;
wire sel;

always_comb
begin
    A_n = A_r; // default;
               // rdt. but safe
    A_n = B_in;

    if (sel)
        A_n = C_in;
end

always_ff @( posedge clk )
begin
    A_r <= A_n;
end
```


What does this do?

For each always_comb, assign, always_ff statement, draw the gates and wires.

```
wire A_n, B_in, C_in;  
reg A_r;  
wire choose;
```

```
always_comb  
begin  
    A_n = A_r; // default  
  
    A_n = B_in;  
  
    if (choose)  
        A_n = C_in;  
end
```
 
```
always_ff @( posedge clk )  
begin  
    A_r <= A_n;  
end
```



Verilog execution semantics

- Confusing
- Best solution is to write synthesizable verilog that corresponds exactly to logic you have *already* designed on paper.
- Debugging is **very** difficult for Verilog. Don't write code and "see if it works." Test each "unknown" thing individually until you know what it does; then combine into larger entities.
- Before you try to simulate, manually check every wire to make sure that it is correctly (1) defined, connected to (2) source and (3) destination, and that (4) the logic driving it appears to be correct.
 - This is *way faster* than finding the same bugs in the waveform viewer!

Verilog struct example

lab 2a examined this

```
typedef struct packed {  
    logic [17-1:0] instr;  
    logic [10-1:0] addr;  
} instr_packet_s;  
  
instr_packet_s ip_n, ip_A_r, ip_B_r, ip_C_r;  
  
assign ip_n = `{addr: addr_i  
               , instr: instr_i};  
  
assign { addr_o, instr_o }  
       = { ip_C_r.addr, ip_C_r.instr };  
  
always_ff @( posedge clk )  
begin  
    { ip_A_r, ip_B_r, ip_C_r } <=  
    { ip_n, ip_A_r, ip_B_r };  
  
end
```